

Part 4 of Extra Material for use with

PSpice[®]
Simulation of Power
Electronics Circuits

A book published by Chapman & Hall, 1997

by R. Ramshaw
ECE Dept.
University of Waterloo.

Contents

- Chapter 10
 - Section 10.4 and Worked EXAMPLE and Extra Drill Exercises

See Appendix E in the book.

© 1997

This material is provided strictly "as-is" for use with the book and is intended for exercises and not for design. The authors and Chapman & Hall specifically disclaim all warranties, express or implied including, but not limited to, implied warranties of merchantability and fitness for a particular purpose. With respect to these extra materials associated with the book and made available on the WEBSITE, the authors and publisher shall have no liability with respect to any loss or damage directly or indirectly arising from the use of these associated materials provided on the WEBSITE. Without limiting the foregoing, the authors and publisher shall not be liable for any loss of profit, interruption of business, damage of equipment or data, interruption of operations or any other commercial damage, including but not limited to, direct, indirect, special, incidental, consequential or other damages.

Do not rent, lease, sell, or publish this material in whole or in part without the express permission of the authors and Chapman & Hall.

10.4 INTEGRAL-CYCLE CONVERTERS

Integral-cycle converters can perform direct ac to ac conversion without intermediate ac-dc, dc-ac conversion and it can be accomplished with lossless switching. See PESS Fig. 1.5.

The basis of integral-cycle control is that a sinusoid can be approximated by combining and removing half cycles from a higher frequency ac source. Since only half or full cycles are ever used, the converter switches are turned on or off only during half-cycle boundaries at which the input voltage passes through zero. As a result, these converters achieve zero-voltage switching without the need for a resonant circuit. This is demonstrated in the following examples.

EXAMPLE W10.4.1

Figure W10.4.1a illustrates a simple integral-cycle controller. This figure comprises the source, the load, and the power switch which performs the conversion. In this particular example we desire to reduce the source frequency by a factor of three. Determine a suitable switching sequence and simulate using PSpice. Display the resulting load voltage using PROBE. Determine the total harmonic distortion THD of the output voltage.

Solution

This is a general example with many free choices for parameter values. There are four steps to achieve a solution.

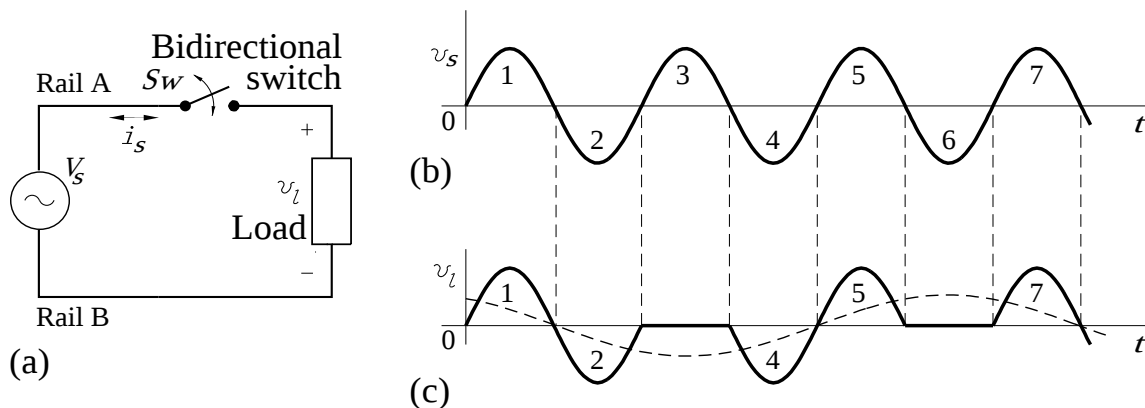


Fig. W10.4.1 Integral-cycle control.

(a) Circuit diagram, (b) source voltage, (c) load voltage.

* SOURCES

```
VS      1 0 SIN(0 {VMAX} {FREQ} 0 0 0)
VSIN   11 0 SIN(0 {3*VMAX} {FREQ/3} 0 0 -240); Sinewave at 1kHz.
VG      10 0 PULSE(0 1V 0 2ns 2ns {PERIOD-4ns} {3*PERIOD/2})
```

* CIRCUIT ELEMENTS

SW	1 2 10 0	SWITCH;	SWITCH parameters in POWER.LIB.
RL	2 0 {RLOAD};		Output load resistance.

* ANALYSIS

. FOUR	1kHz	15 v(2);	Fourier analysis of output waveform.
. TRAN	5us	2ms;	Two load cycles.
. PROBE			
. END			

[illegible]

STEP 3

The third step is to run the PSpice program with the circuit file W10_4_1.CIR.

STEP 4

STEP 4 The fourth step is to run PROBE with W10_4_1.DAT and view the results. See Fig. W10.4.1e. The load voltage is an alternating voltage source missing every third half-cycle of the supply waveform. The load voltage distortion of 170.3% is obtained from EX10_4_1 .OUT.

 


Fig. W10.4.1e

END OF EXAMPLE W10.4.1

Drill Exercise WD10.4.1

Consider EXAMPLE W10.4.1 and add a parallel inductance $100\mu\text{H}$ to the existing load resistance. Simulate using PSpice and plot the resulting load- resistance current and the inductor current.

Drill Exercise WD10.4.1a

Consider the ac-ac converter illustrated in Fig. W10.4.1a. The circuit has the following specifications.

$V_s = 50\text{V(rms)}$ at 200kHz , bidirectional switch, $R_l = 5\Omega$.


Load-voltage frequency 40kHz (symmetrical waveform).

Follow the pattern of EXAMPLE W10.4.1 and do a PSpice simulation. Plot traces of the supply and the load voltages. Determine **(a)** the rms value of the load voltage, **(b)** the fundamental rms value of the load voltage and **(c)** the total harmonic distortion THD of the load-voltage waveform.

(Ans: **(a)** 31.6V , **(b)** 7.77V , **(c)** 393.0% .)

The previous example was a simple introduction to the concept of integral-cycle converters. Since all switching occurs during the zero-crossing of the source voltage there should be lossless switching. Also, this technique results in a load-voltage waveform with substantial distortion and a reduced voltage. Because only a single switch is used in EXAMPLE W10.4.1, there are significant limitations to its use.

Fig. 10.4.1
Single-phase ac-ac converter.

 

The flexibility of an integral-cycle converter may be enhanced if four switches are used in a bridge configuration, as illustrated in Fig. 10.4.1. As before, the load-voltage waveform is constructed using half-cycles from the ac source, but the bridge provides the added ability to reverse the polarity of any half-cycle. In the figure, a resonant LC circuit is shown across the input source. It is tuned to the

source frequency to filter out any noise, interference, or distortion which may be present in a practical implementation. This may be necessary since any superimposed noise on the ac source could cause non-zero voltage switching.

EXAMPLE W10.4.2

An integral half-cycle converter, using four switches in a bridge configuration, is illustrated in Fig. 10.4.1. Use this topology to convert an input ac source with a voltage of 500V and a frequency of 5kHz into a load requiring a frequency of roughly 385Hz. Use a resistive load of 10ohms and assume the source impedance is negligible. In this case it may be assumed that the input source is free of noise and harmonics so that the input LC filter is unnecessary. Develop the driver scheme and use PSpice to simulate this circuit. Use PROBE to display the resulting load voltage. Determine **(a)** the total rms and fundamental rms values of the load voltage and **(b)** the total harmonic distortion THD of the load-voltage waveform.

Solution

There are four steps to achieve a solution.

STEP 1

The first step is to transform the circuit diagram into PSpice elements and nodes. The resulting configuration is illustrated in Fig. W10.4.2a.

 


Fig. W10.4.2a Single phase ac-converter configuration.

STEP 2

The next step is to transform the configuration in Fig. W10.4.2a into a PSpice circuit file. The ratio of the input frequency f_s to output frequency f_l is

$$f_s/f_l = T_l/T_s = 5000/385 \approx 12.987.$$

Since the output waveform must be constructed using some combination of half cycles, the output period must be an integer multiple of the input period. In this case we will round up to an integer multiplier of 13. During each 13 input cycles there are potentially 26 half-cycles which may be used to construct a new alternating waveform close to the required output frequency. A pattern, whereby a sinusoid is approximated by varying the number of clustered half-cycles, is required. One possible switching sequence is illustrated in Fig. W10.4.2b.

In this particular case, with an odd number of input cycles (13) per half cycle of the output voltage, the switches can be bidirectional. In this way, the gate signals have the same pattern each half cycle of the output, but the load-voltage polarity changes each half cycle.

From Fig. W10.4.2b we see that the gate control for this type of converter is quite complex. The controller is required to give an unevenly spaced series of precisely placed pulses. The switch control voltage is not a regular periodic squarewave, so it is best realized in PSpice by using the enhanced piecewise linear source (PWL).

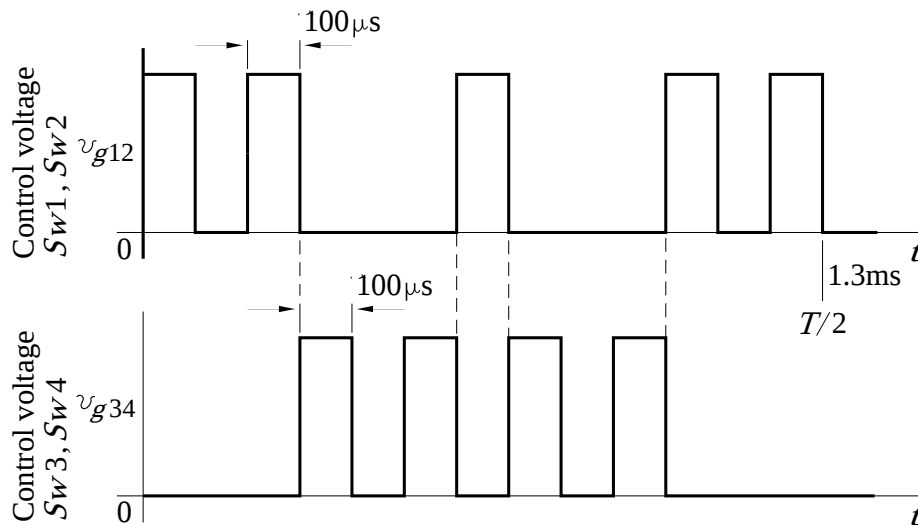


Fig. W10.4.2b Switch control sequence.

HIGH-FREQUENCY INTEGRAL HALF-CYCLE AC-AC CYCLOCONVERTER

. LIB POWER.LIB

Convergence aid.

```
.PARAM FREQ=5kHz
```

Source resistance.

* SOURCE and LOAD

```
RS 10 1 {RESOURCE}
```

```
VG12 20 0 PWL REPEAT FOREVER
```

```
+ 300us,0 600us,0 600.01us,1 699.99us,1 700us,0
```

```
+ 1200.01us,1 1300us,1    ENDREPEAT
```

```
+ 0,0 300us,0 300.01us,1 399.99us,1 400us,0 500us,0
```

```
+ 799.99us,1 800us,0 900us,0 900.01us,1 999.99us,1
```

```
+ 1000us,0 1300us,0  ENDREPEAT
```

```
SW1 1 2 20 0 SWITCH
```

SW3 1 3 21 0 SWITCH

```
RL  2  3  {RLOAD};
```

Output load resistance.

* A time-step ceiling is used to increase the plot resolution.

```
.TRAN          5us 3.9ms 0      4us
```

Source and load voltages.

[illegible]

The third step is to run the PSpice program with the circuit file W10 4 2.CIR.

STEP 4

The fourth step is to run PROBE and view the results which are displayed in Fig. W10.4.2c.

Part (a) of Solution. From PROBE and the file W10_4_2.OUT the load voltages are $V_{l\text{rms}} = 411.8\text{V}$ and $V_{l1\text{rms}} = 281.4\text{V}$.

Part (b) of Solution. From the output file W10_4_2.OUT, the total harmonic distortion THD of the output-voltage waveform is $\text{THD} = 88.57\%$. Compare this with EXAMPLE 10.4.1.

 


Fig. W10.4.2c

END OF EXAMPLE W10.4.2

Drill Exercise WD10.4.2

Consider EXAMPLE W10.4.2 and modify the circuit file to use a source frequency of 13kHz and an output frequency of 1kHz. Display the load voltage using PROBE. Determine (a) the average power absorbed by the load and (b) the total harmonic distortion THD of the load-voltage waveform.

